
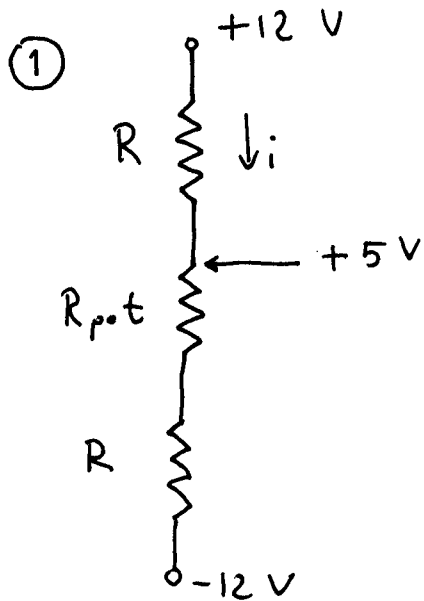


# ME333 Introduction to Mechatronics

## Assignment 1

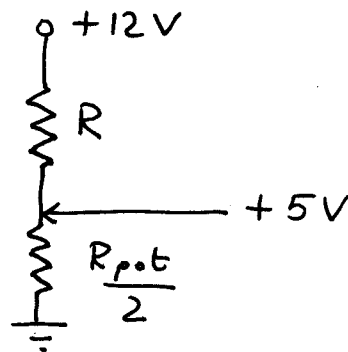

Due to symmetry, this circuit equals



voltage divider:

$$\frac{5}{12} = \frac{\left(\frac{R_{pot}}{2}\right)}{R + \left(\frac{R_{pot}}{2}\right)}$$

yielding


$$R = 0.7 R_{pot}$$

Current:  $12 = Ri + 5 \Rightarrow i = \frac{7}{R} = \frac{10}{R_{pot}}$

Total resistance:  $R_T = 2R + R_{pot} = 2.4 R_{pot}$

Power dissipated:  $P = i^2 R_T = \frac{240}{R_{pot}}$

②

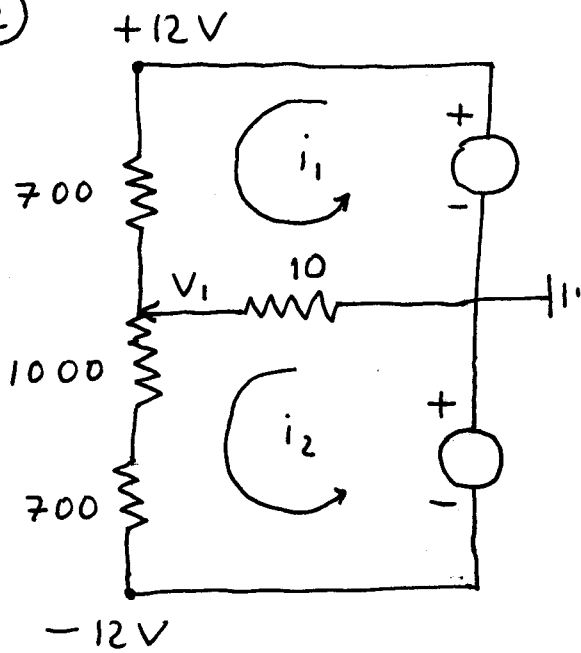

Equations:

$$12 = 700 i_1 + V_1$$

$$V_1 = 1700 i_2 - 12$$

$$V_1 = 10 (i_1 - i_2)$$

Arranging terms,

$$V_1 + 700 i_1 = 12$$

$$V_1 - 1700 i_2 = -12$$

$$V_1 - 10 i_1 + 10 i_2 = 0$$


Solving the system,

$$V_1 = 0.09885 \text{ V}$$

$$\text{also, } i_1 = 17.0 \text{ mA}$$

$$i_2 = 7.11 \text{ mA}$$


Wiper at bottom:

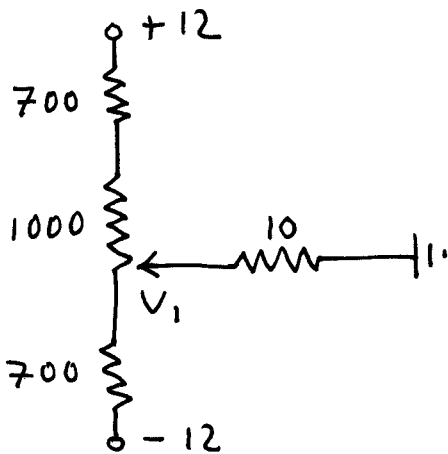

again using symmetry,

$$V_1 = -0.09885 \text{ V}$$

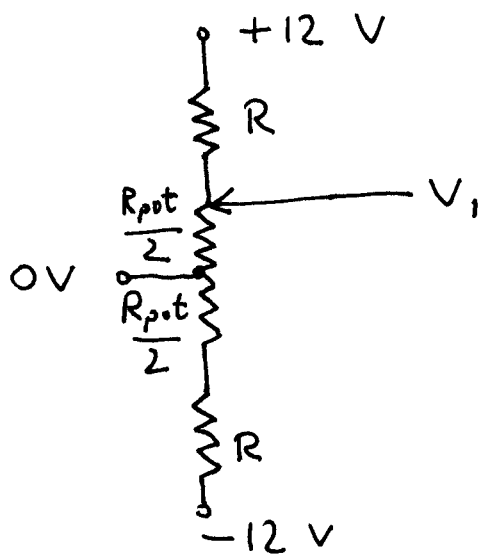
③ Without load, the circuit is a simple voltage divider.  $V_1$  is our "signal"; when the wiper is at the top, we have



$$V_1 = \frac{\frac{R_{pot}}{2}}{R + \frac{R_{pot}}{2}} (12)$$

$$V_1 = 12 \frac{R_{pot}}{2R + R_{pot}}$$

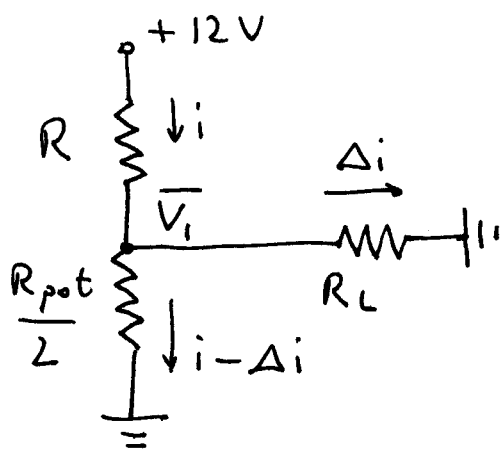when we load the circuit with  $R_L$ , the above expression for  $V_1$  no longer holds:



let's find  $\bar{V}_1$ :

$$12 = Ri + \bar{V}_1$$

$$\bar{V}_1 = R_L \Delta i$$

$$\bar{V}_1 = \frac{R_{pot}}{2} (i - \Delta i)$$

After some manipulation we obtain

$$\bar{V}_1 = 12 \frac{R_{pot}}{2R + R_{pot} + \frac{R R_{pot}}{R_L}}$$

the last term in the denominator,  $\frac{R R_{pot}}{R_L}$ , causes  $\bar{V}_1$  to be smaller than the desired value  $V_1$ . The lower the load impedance,  $R_L$ , the greater the difference between  $\bar{V}_1$  and  $V_1$ .

We could reduce the effect of the term  $\frac{RR_{pot}}{R_L}$  by reducing  $R$  or  $R_{pot}$ .

However, the power dissipated by the unloaded circuit is

$$P = \frac{(12 - (-12))^2}{2R + R_{pot}} = \frac{576}{2R + R_{pot}}$$


in consequence, reducing  $R$  or  $R_{pot}$  will increase power dissipation

④ Let's call the  $10\ \Omega$  resistor  $R_L$ ;


$h_{FE} \equiv$  transistor current gain = 100

The equivalent impedance of the amplifier with load is  $Z_{in} = (h_{FE} + 1)R_L = 1010\ \Omega$

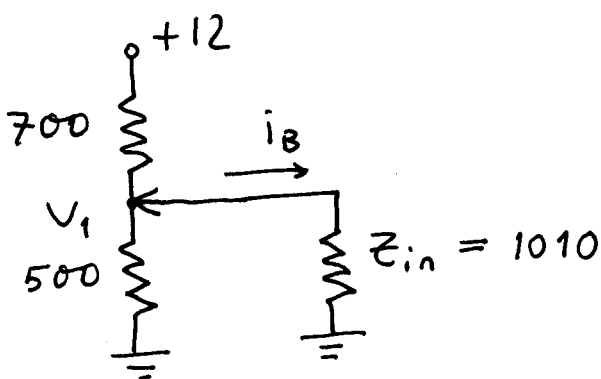$\therefore$  an equivalent circuit would be



OR

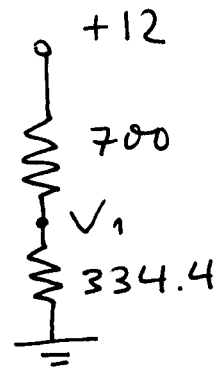

$$\therefore V_1 = \frac{334.4}{700 + 334.4} (12) = 3.88\text{ V}$$

$$i_B = \frac{V_1}{Z_{in}} = \frac{3.88\text{ V}}{1010\ \Omega} = 3.84\text{ mA}$$

$V_{OUT}$ : the base-emitter junction typically has a "conducting diode" voltage drop  $V_{BE}$  of about 0.6 V


thus  $V_{OUT} = V_1 - V_{BE} \approx 3.28 \text{ V}$

The amplifier is not ideal because:

a) The input impedance  $Z_{in}$  is not large enough; it still loads the control circuit considerably, causing  $V_1$  to be 3.88 V instead of the desired 5V.

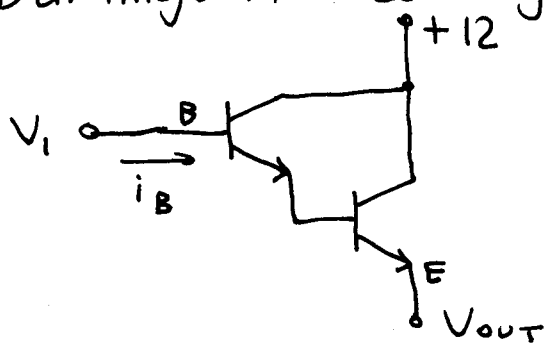b) The base-emitter voltage drop means that the amplifier will turn off whenever  $V_1 < V_{BE}$ .

The amplifier could be improved by increasing the current gain (hence increasing  $Z_{in}$ ). This could be achieved by cascading two transistors (Darlington configuration):



now  $Z_{in} = (h_{FE} + 1)^2 R_L$   
 however at the cost of increasing deadband  
 $(V_{BE} \approx 1.2 \text{ V})$

Wiper at bottom-most position: (current flows right to left: +12

